

Lab Report 3.1

Date: 7th September 2021

Name: Rita Abani

Roll No: 19244

Title of Experiment: Objective 3.1 : For the given RLC circuit, apply input signals of different frequencies and vary the resistance values for a fixed value of L and C and measure output voltage, $V_{out}(t)$.

Brief Description:

In this experiment, we had to simulate RLC circuits with a sinusoidal input source and AC analysis on LTSpice and then take note of the Voltages across the capacitor with time graphically. The series RLC circuit is composed of an inductor (L) and resistor (R) and capacitor (C) in series along with an input signal with variable frequencies (1Hz-10MHz). Instead of analysing each passive element separately, we can combine all three together into a series RLC circuit. The analysis of a **series RLC circuit** is the same as that for the dual series R_L and R_C circuits we looked at previously, except this time we need to take into account the magnitudes of both X_L and X_C to find the overall circuit reactance. Series RLC circuits are classed as second-order circuits because they contain two energy storage elements, an inductance L and a capacitance C

Schematic diagram:

In our circuit, we consider the following settings for the Independent Voltage Source:

Independent Voltage Source - V1

Functions

☐ (none)

☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

☒ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)

☐ SFFM(Voff Vamp Fcar MDI Fsig)

☐ PWL(t1 v1 t2 v2...)

☐ PWL FILE: Browse

DC offset[V]:

Amplitude[V]:

Freq[Hz]:

Tdelay[s]:

Theta[1/s]:

Phi[deg]:

Ncycles:

Additional PWL Points

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒

Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic: ☒

Cancel OK

We then use AC analysis of Decade Type with a 1000 points per decade starting from 1Hz- to 10MHz to simulate the circuit.

Edit Simulation Command

Transient AC Analysis DC sweep Noise DC Transfer DC op pnt

Compute the small signal AC behavior of the circuit linearized about its DC operating point

Type of sweep:

Number of points per decade:

Start frequency:

Stop frequency:

Syntax: .ac <oct, dec, lin> <Npoints> <StartFreq> <EndFreq>


.ac dec 1000 1 10M

Cancel OK


We considered experimenting with the following 3 RLC circuit setups:

Cases

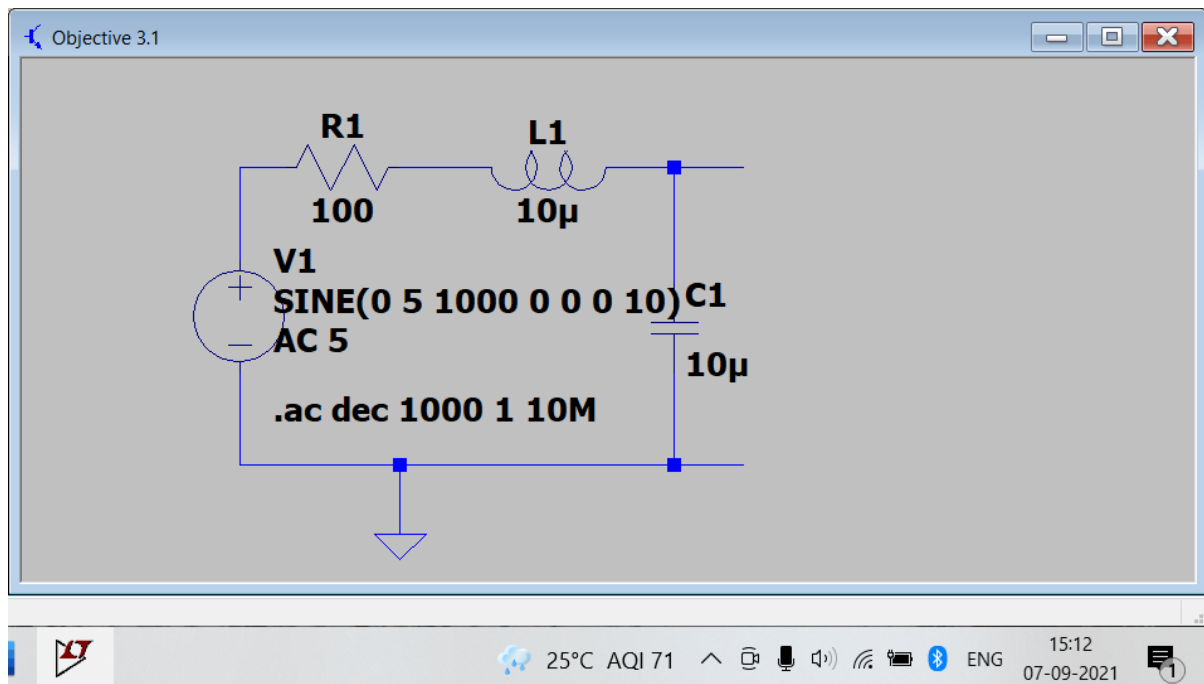
1) $R=100\Omega$; $L=10\mu\text{H}$; $C=10\mu\text{F}$



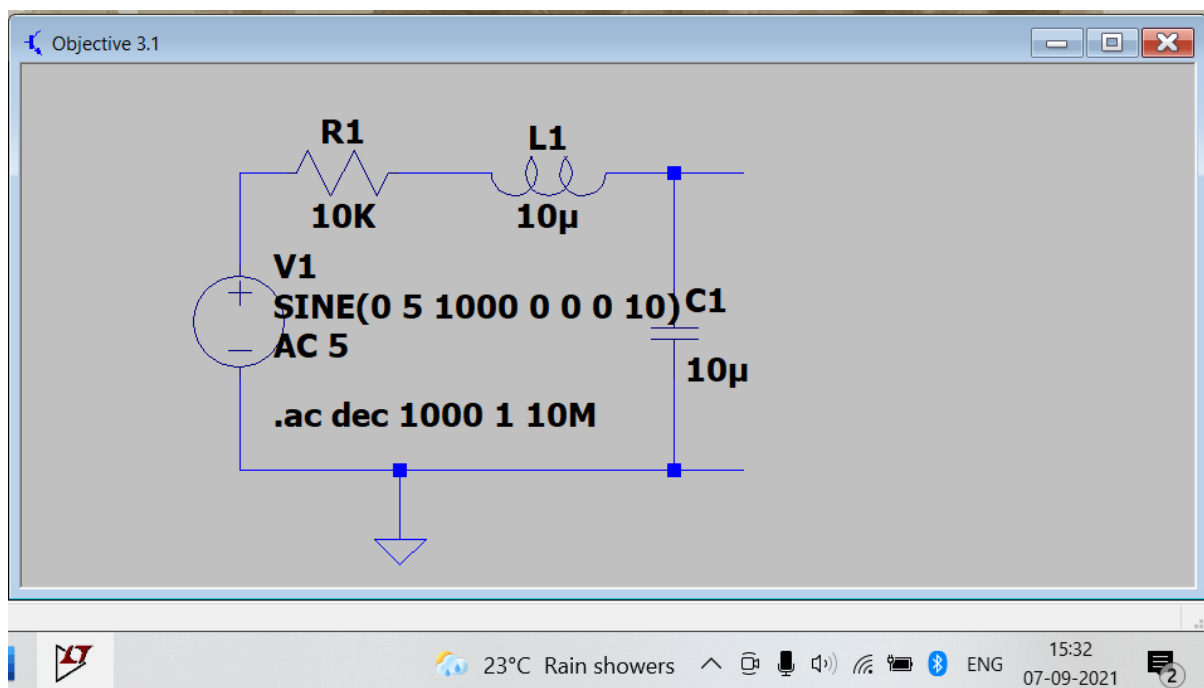2) $R=10\text{K}\Omega$; $L=10\mu\text{H}$; $C=10\mu\text{F}$



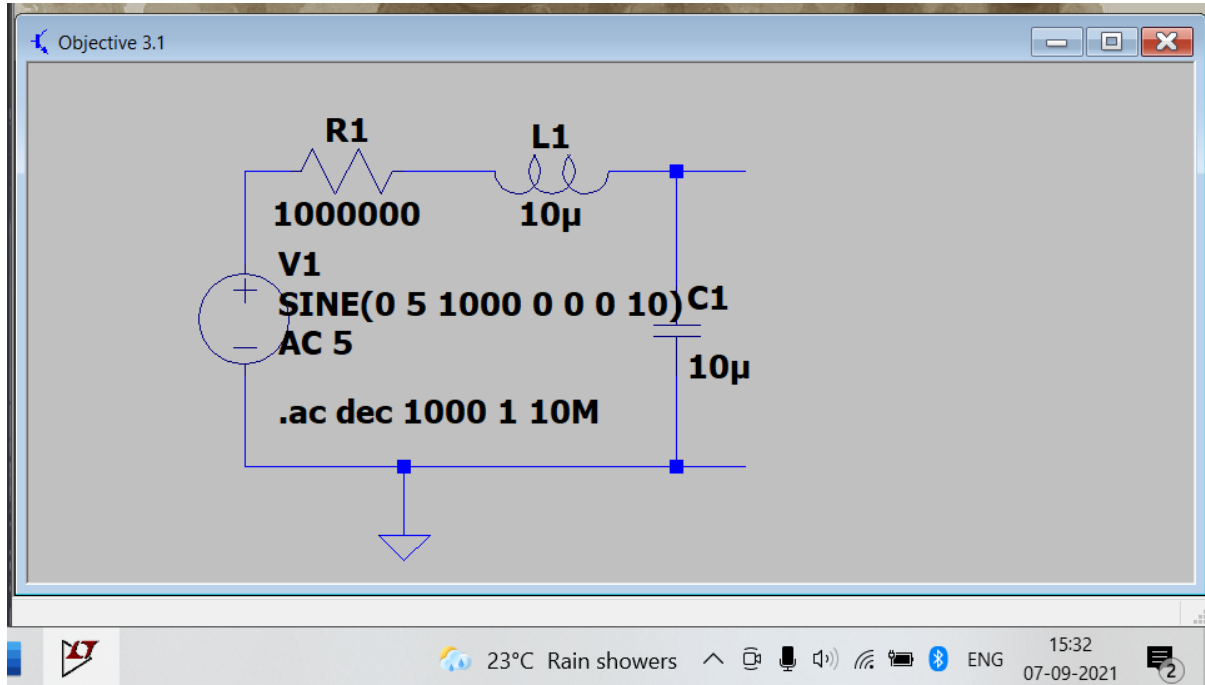3) $R=1M\Omega$; $L=10\mu H$; $C=10\mu F$




Results:


S.No	Resistance (in Ω)	Capacitance(in μF)	Inductance(in μH)
1	100	10	10
2	10000	10	10
3	1000000	10	10

The graphs obtained corresponding to each of the above cases are as follows :


1)

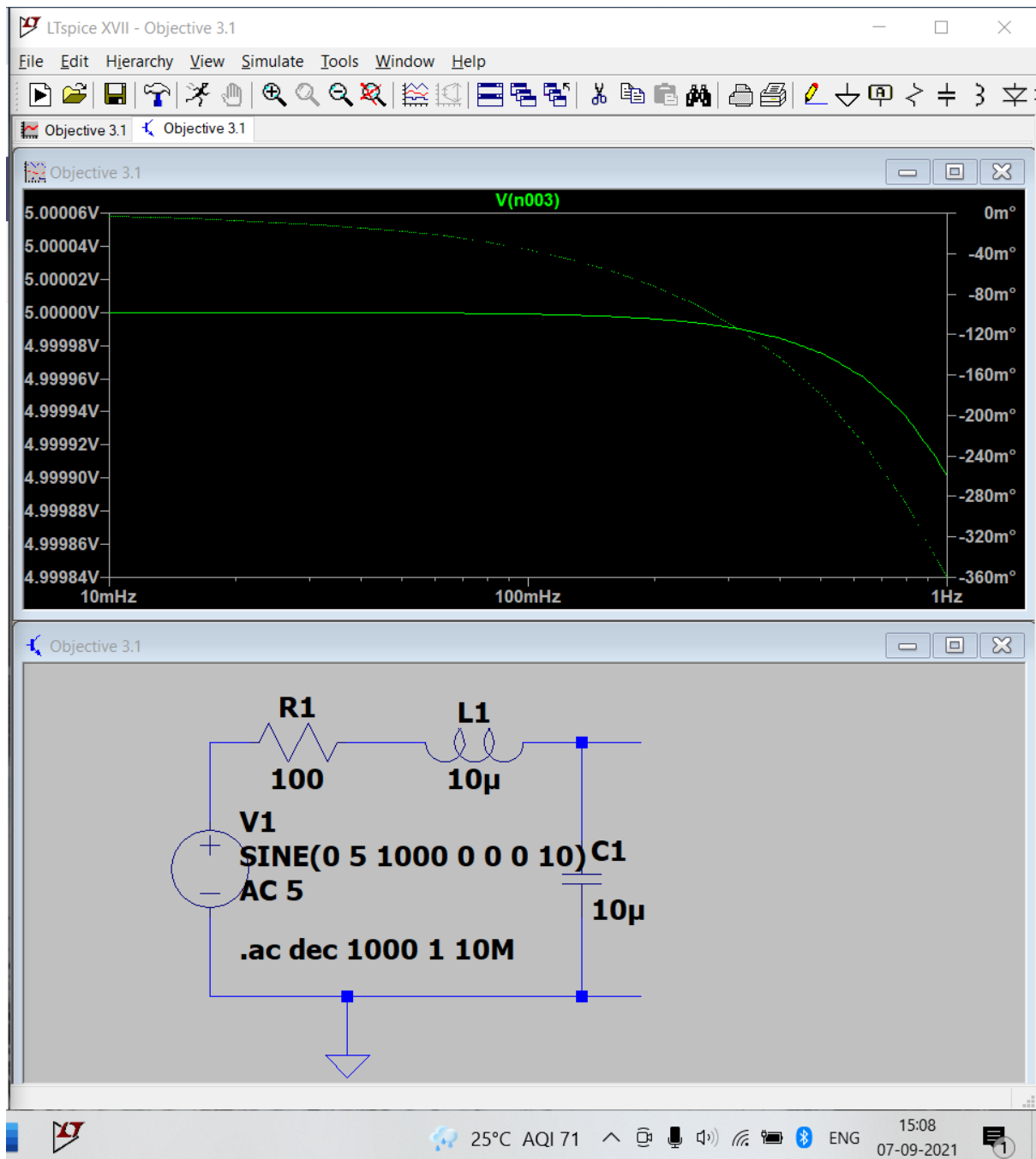

2)

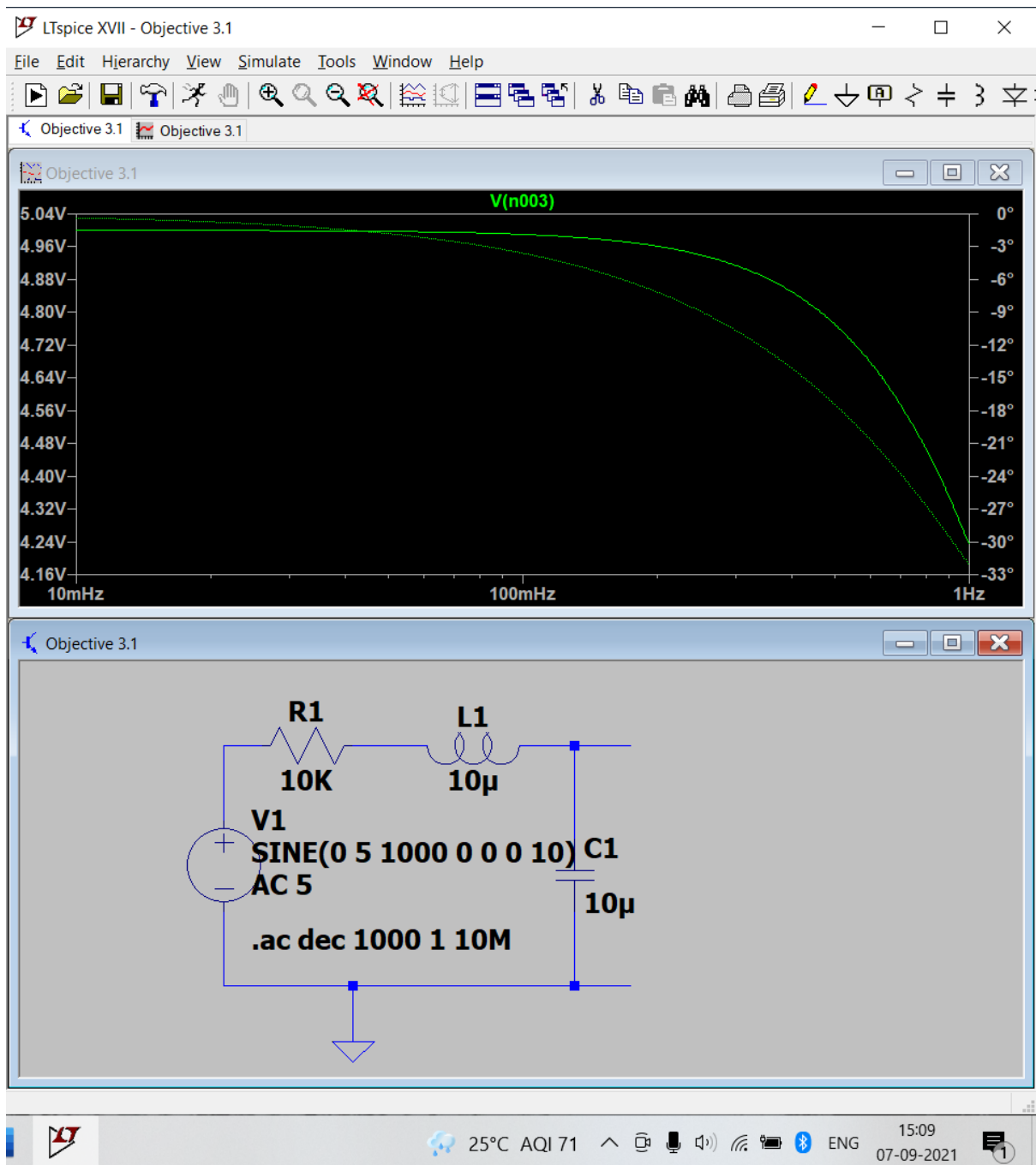

3)

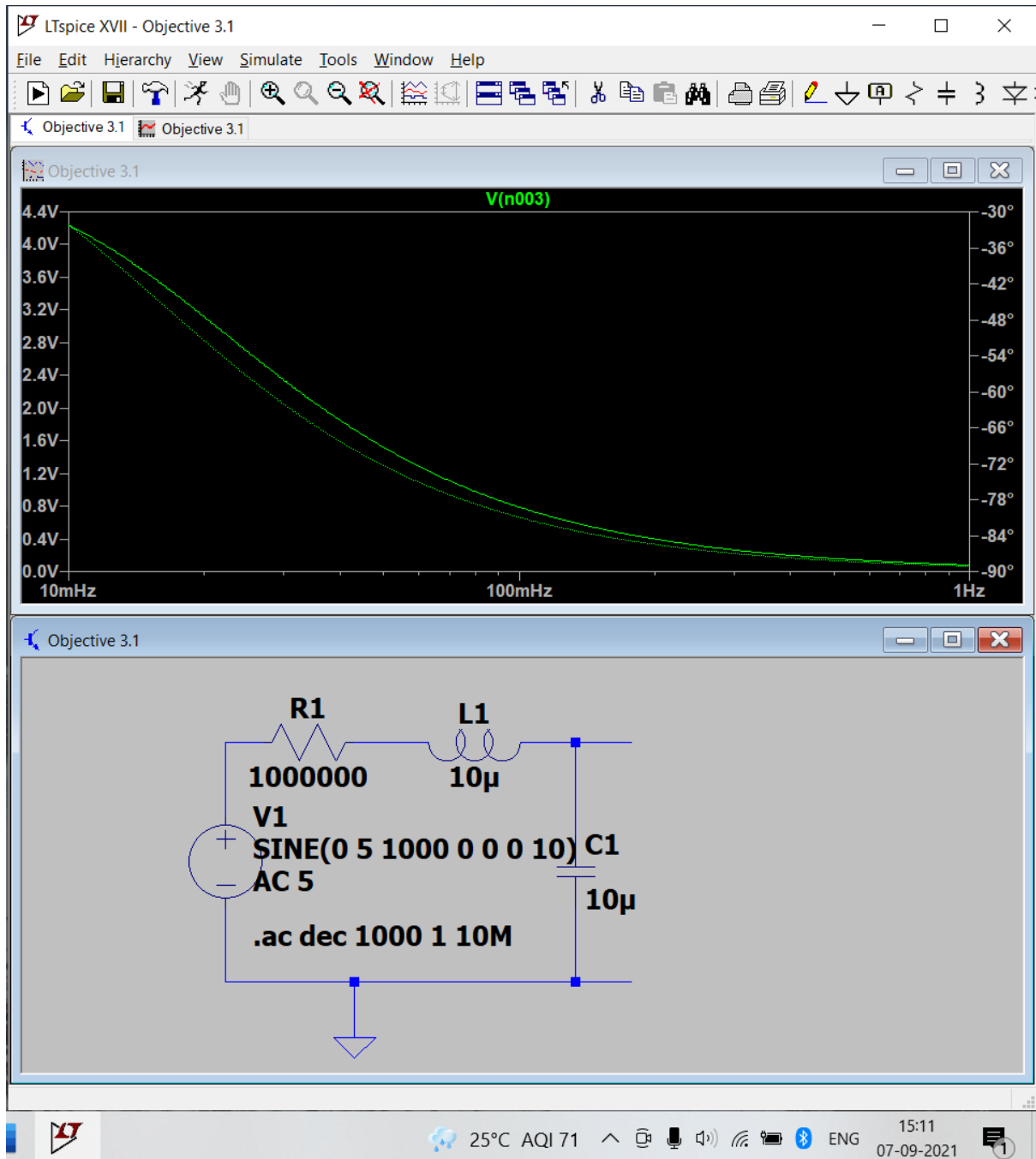

Discussion:

The following table helps us intuitively understand waveforms and bode plots so obtained.

Element	Resistance	Reactance(X)	Impedance(Z)
Resistor	R	0	$Z=R$
Inductor	0	ωL	$Z = j\omega L$
Capacitor	0	$1/\omega C$	$Z=1/(j\omega C)$

In case of pure ohmic resistors, the voltage and current waveforms are in phase with each other. In a pure inductor, the voltage waveform leads the current by 90 degrees and in case of a capacitor, the voltage lags current by 90 degrees. This phase difference depends on the reactive value of the components being used as can be seen from the table above.

The RLC circuit helps us analyze each of the circuit elements simultaneously. Contrary to the RC and RL circuits, in this circuit, we considered L and C together while calculating the overall circuit's reactance. This setup being a series circuit, had the same current flowing through each of the elements. We conclude that since reactances of L and C are a function of frequency as can be seen from the table above, hence the sinusoidal response of the circuit happens to vary with input frequency (which can also be inferred from the Bode Plots in terms of output voltage and phase). Additionally, the individual voltage drop of each of the circuit elements will be out of phase with each other.