

## LAB REPORT FOR EXPERIMENT 1.2

**Date:** August 10, 2021


**Name:** Rita Abani

**Roll No:** 19244

**Title of Experiment: Objectives 1.2: I-V Characteristics of Ohm's Law involving AC Input**

### Brief Description:

This lab session involved the use of LTspice which is an analog electronic circuit simulator computer software, to perform some basic simulations namely first drawing the circuit that involved a resistor of 1K Ohms with an AC voltage source in series. The AC voltage source had the following parameters:

 Independent Voltage Source - V1

Functions

☐ (none)

☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

☒ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)

☐ SFFM(Voff Vamp Fcar MDI Fsig)

☐ PWL(t1 v1 t2 v2...)

☐ PWL FILE:


DC offset[V]:	<input type="text" value="0"/>
Amplitude[V]:	<input type="text" value="8"/>
Freq[Hz]:	<input type="text" value="30"/>
Tdelay[s]:	<input type="text" value="0.1"/>
Theta[1/s]:	<input type="text" value="0"/>
Phi[deg]:	<input type="text" value="0"/>
Ncycles:	<input type="text" value="10"/>

Make this information visible on schematic: ☒

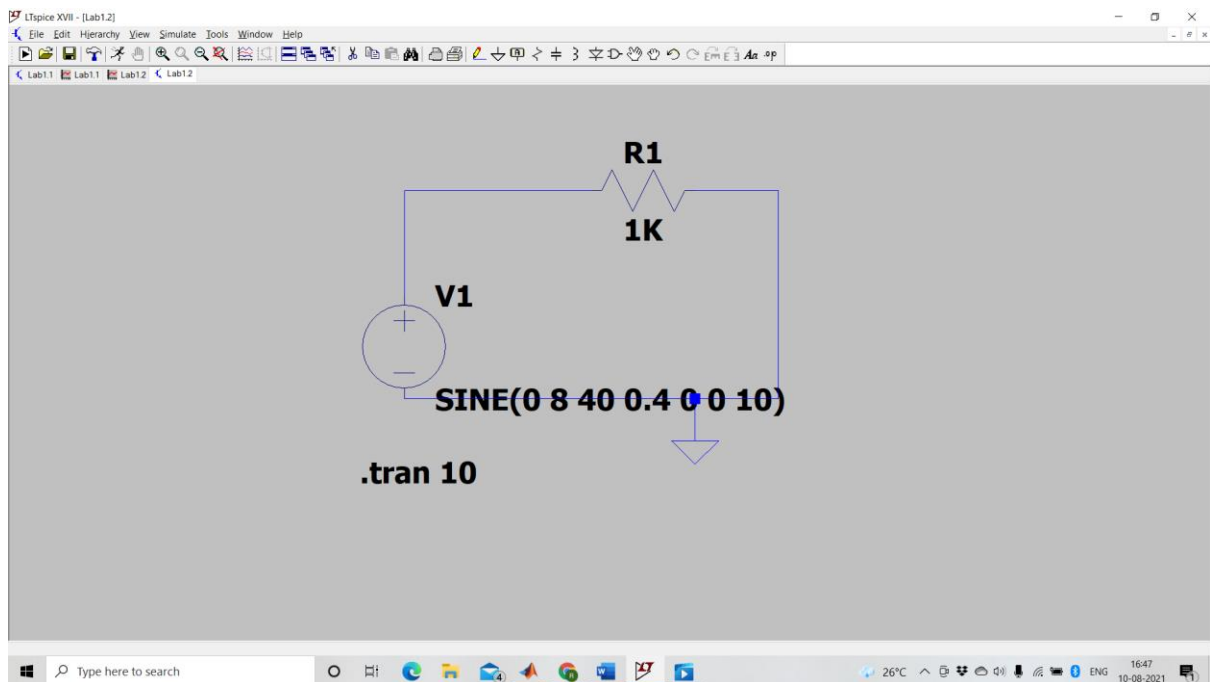
## Schematic diagram:

The following screenshot depicts the circuit setup.


While running the simulations, I tried the AC input with two sets of values as outlined in the results and in the brief procedure above.



## Results:

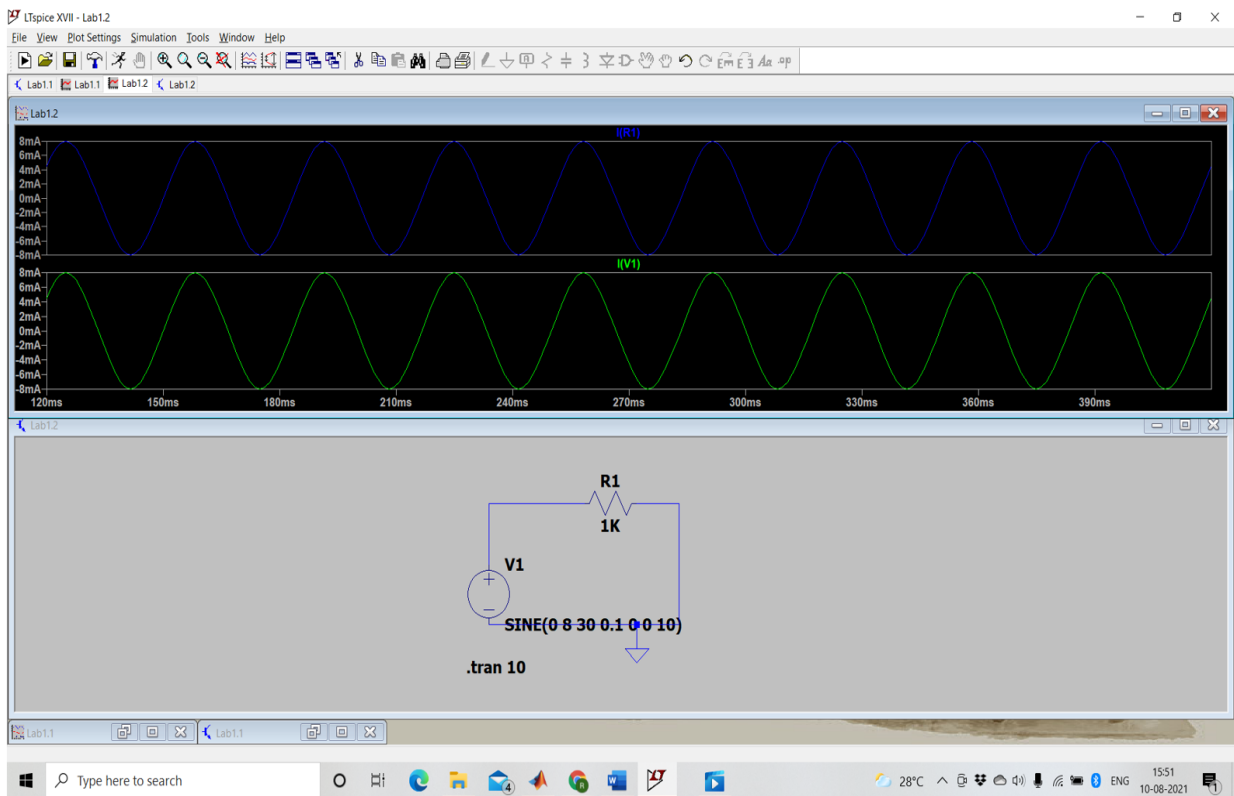

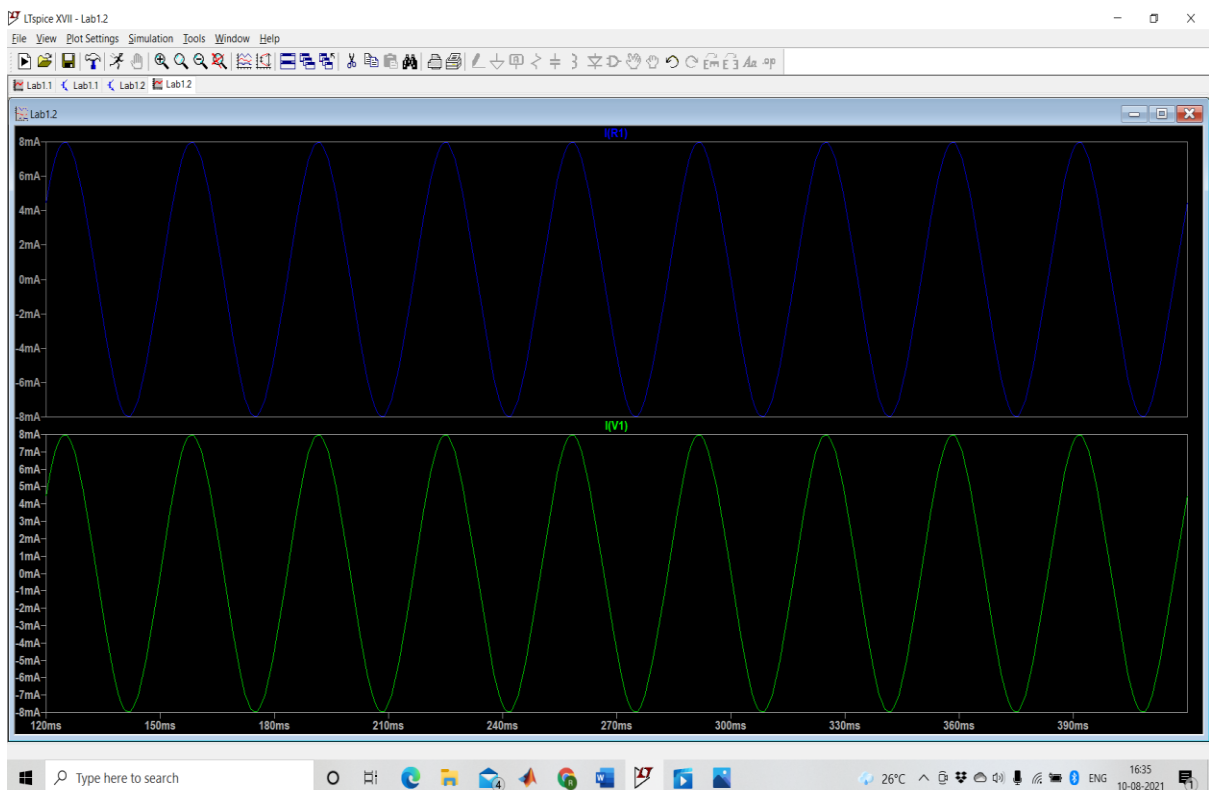An enlarged image of the above is as follows :



This experiment was also performed with another set of values for the AC voltage source:



Independent Voltage Source - V1

Functions

☐ (none)

☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

☒ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)

☐ SFFM(Voff Vamp Fcar MDI Fsig)

☐ PWL(t1 v1 t2 v2...)

PWL FILE:

Browse

DC offset[V]:

0

Amplitude[V]:

8

Freq[Hz]:

40

Tdelay[s]:

0.4

Theta[1/s]:

0

Phi[deg]:

0

Ncycles:



10

Additional PWL Points

Make this information visible on schematic:

☒

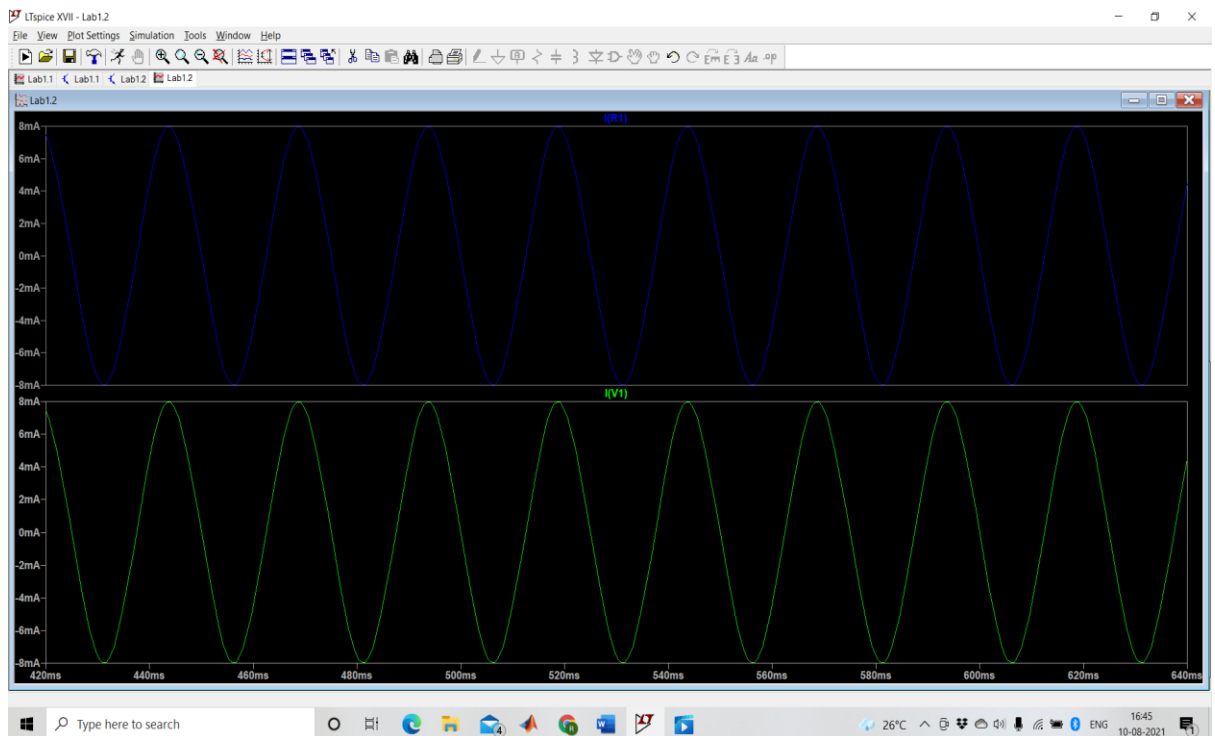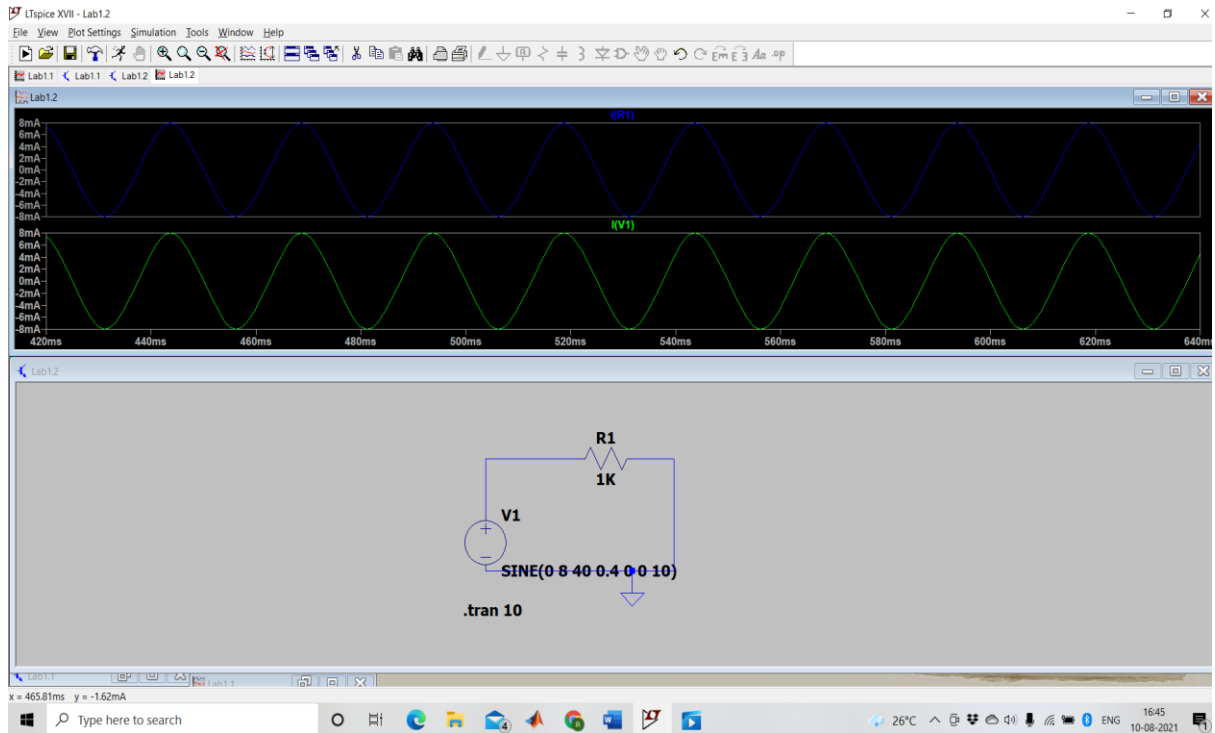The corresponding result obtained is as follows :



**Discussion:**

In this version of performing Experiment 1, the input was generated through an AC voltage source. In real life, a typical AC source is basically an electric generator in which the rotor in a magnetic field generates sine waves as it rotates. So in an AC voltage source, the polarity of the positive and negative terminals change periodically while in the case of a DC source, polarity remains the same.

In an AC circuit, this can be mathematically represented as follows :

$$\Delta V = \Delta V_1 \sin(\omega t)$$

Where  $\Delta V$  is instantaneous voltage ,  $\Delta V_1$  is the maximum voltage of the generator and  $\omega$  is the angular frequency of the AC voltage source.

Ohm's law is applicable to circuits involving an AC voltage source too and is generally written as  $I = V/Z$  where  $Z$  is the impedance of the circuit.

**Hence the Plots we obtained above are in tandem with Ohm's Law**