

Lab Report 4.3

Date: 5th October 2021

Name: Rita Abani

Roll No: 19244

Title of Experiment: Objective 4.3: Study of Clipper and clamper circuit.

Brief Description:

In this experiment, we simulated a circuit in LTSpice to depict the output waveforms of the clipper and clamper circuits. Clipping circuits are used to remove a part of a signal which is above or below a reference level. A clamper circuit, on the other hand, shifts a signal to a defined value. Basically, this circuit adds a DC component to the input signal. Clipping circuits are also known as limiters, amplitude selectors, or slicers. Half-wave rectifier is also a good basic example of clipper circuit where the reference level is zero and the signal below zero voltage (i.e. negative) are not allowed to pass through.

Schematic diagram:

We examine the following two set-ups (including reversing the polarity of the diodes)

Independent Voltage Source - V1

Functions

- ☐ (none)
- ☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- ☒ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- ☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- ☐ SFFM(Voff Vamp Fcar MDI Fsig)
- ☐ PWL(t1 v1 t2 v2...)
- ☐ PWL FILE: Browse

DC offset[V]:

Amplitude[V]:

Freq[Hz]:

Tdelay[s]:

Theta[1/s]:

Phi[deg]:

Ncycles:

Additional PWL Points

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒



Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:


Make this information visible on schematic: ☒

Cancel OK

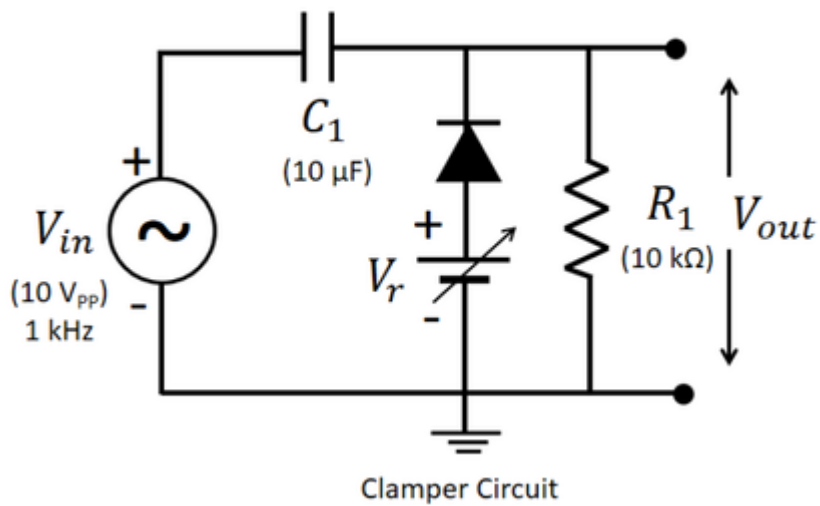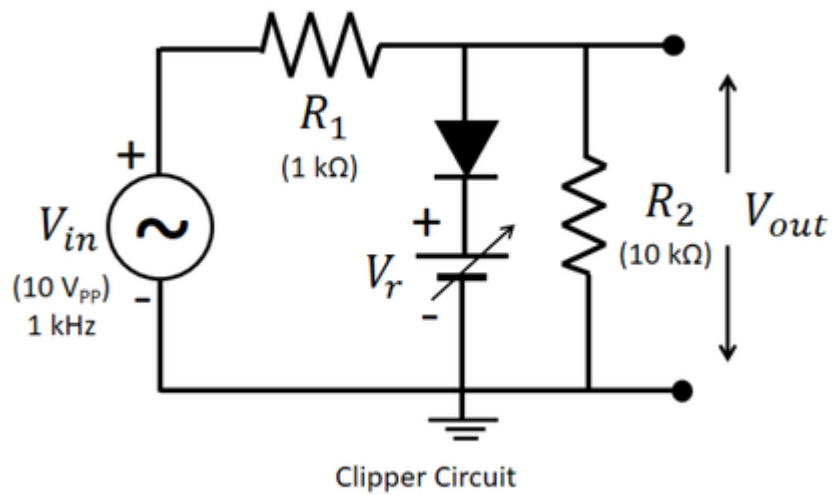


Following are the set-ups we considered:


Case 1: Clipper Circuit

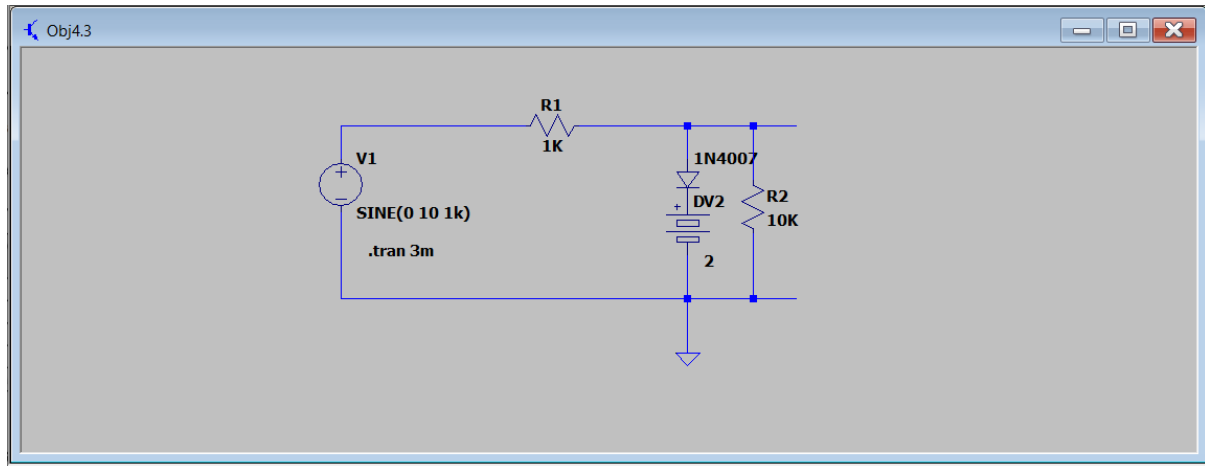


Case 2: Clipper circuit with reversed diode

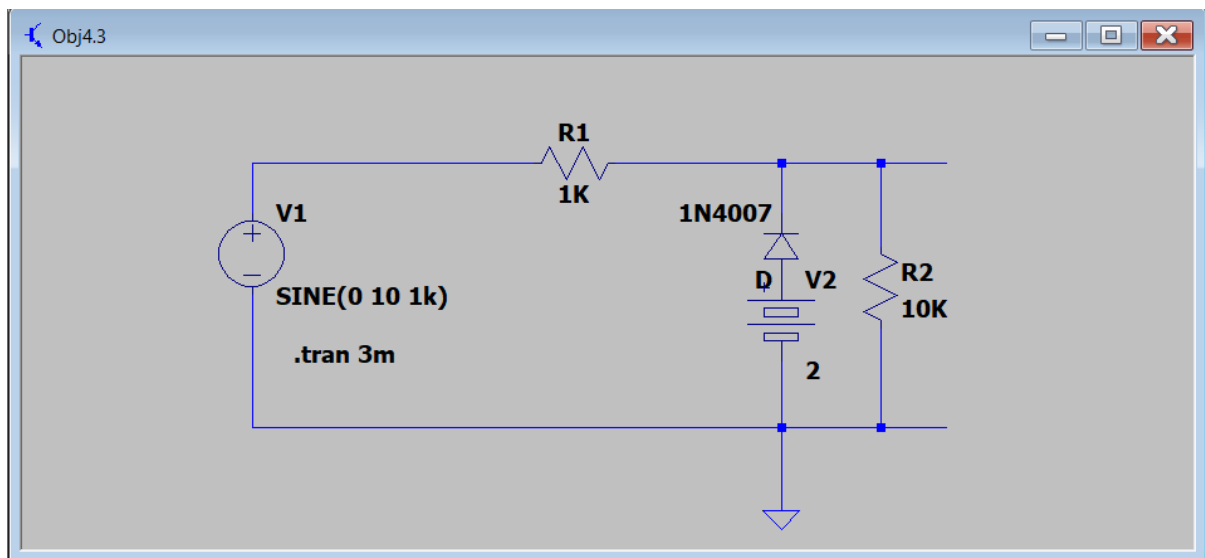

Case 3: Clamper circuit

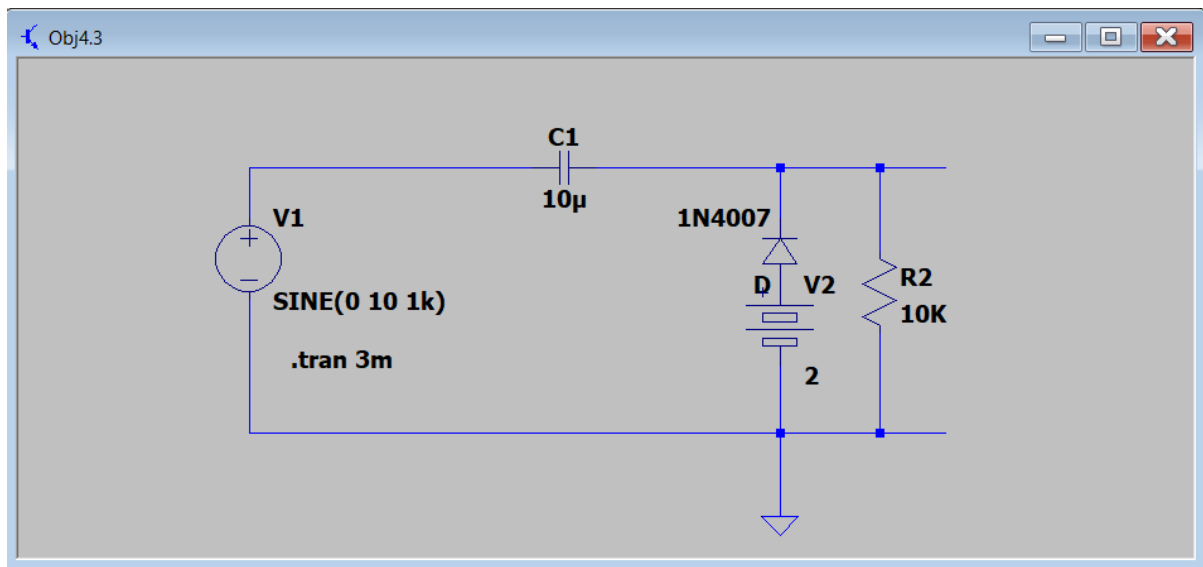

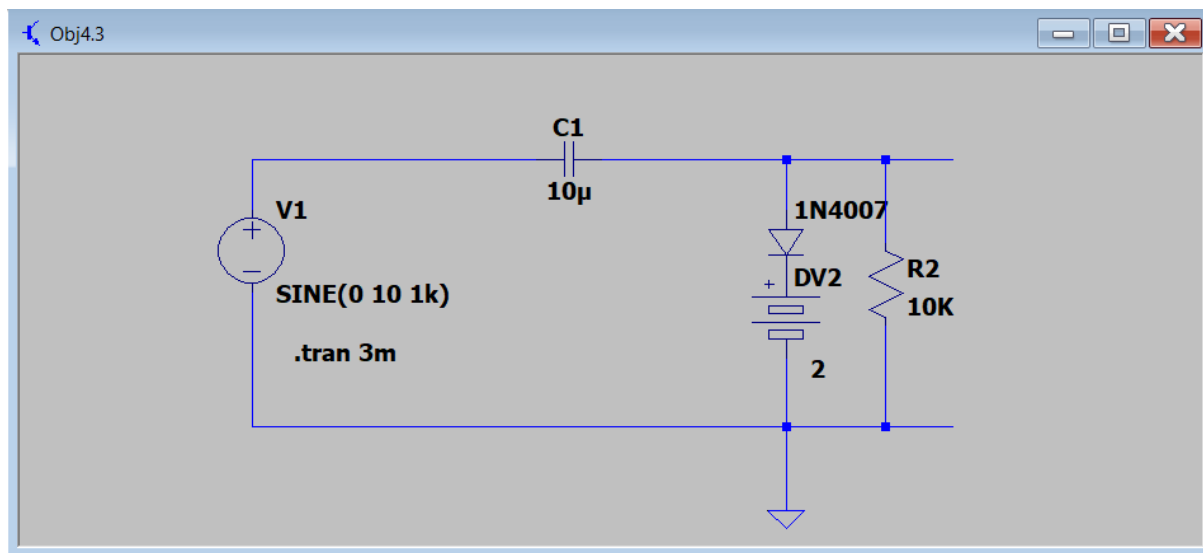
Case 4: Clamper circuit with polarity reversed




Results:

The following are the output clippings of waveforms obtained corresponding to the above cases.


Case 1:

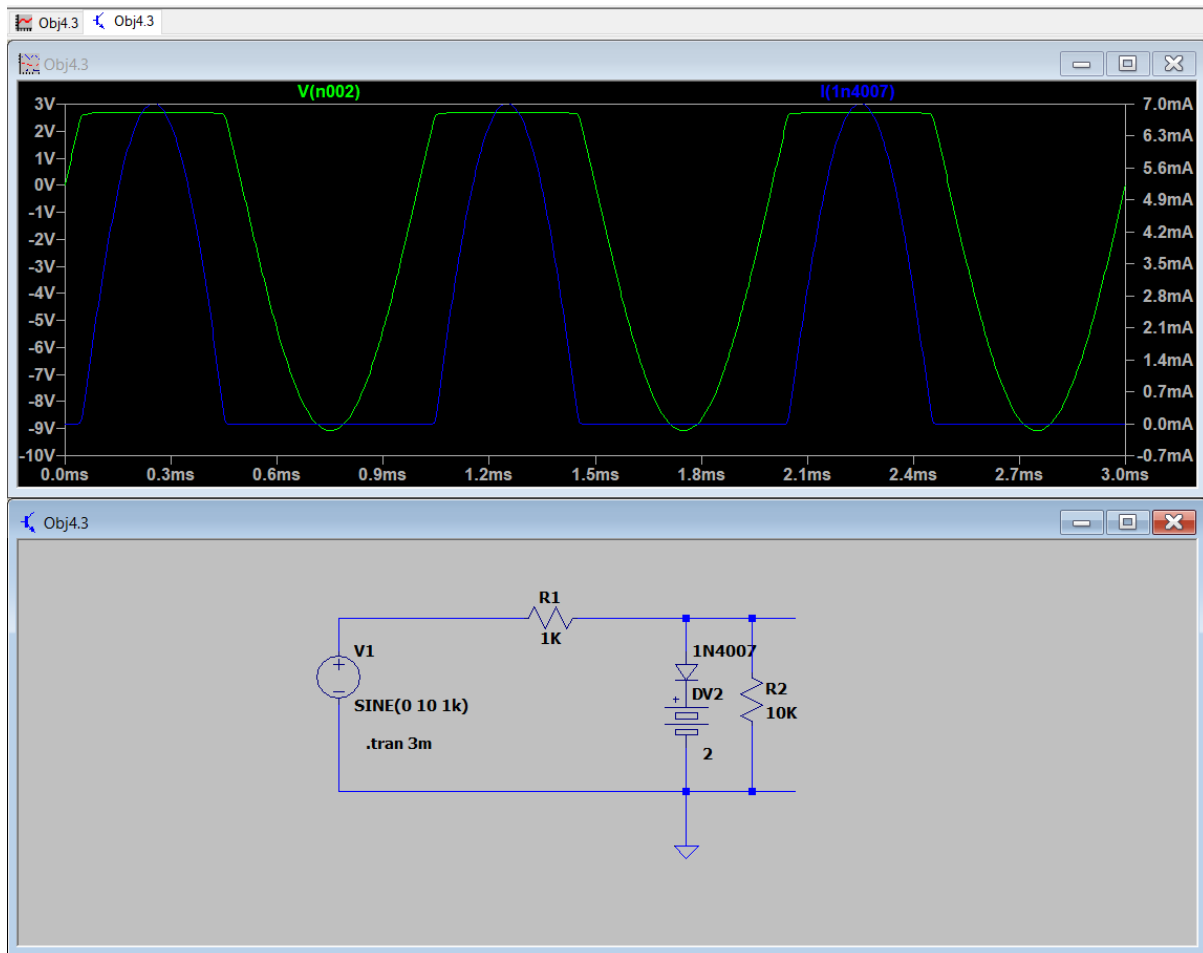


Case 2:

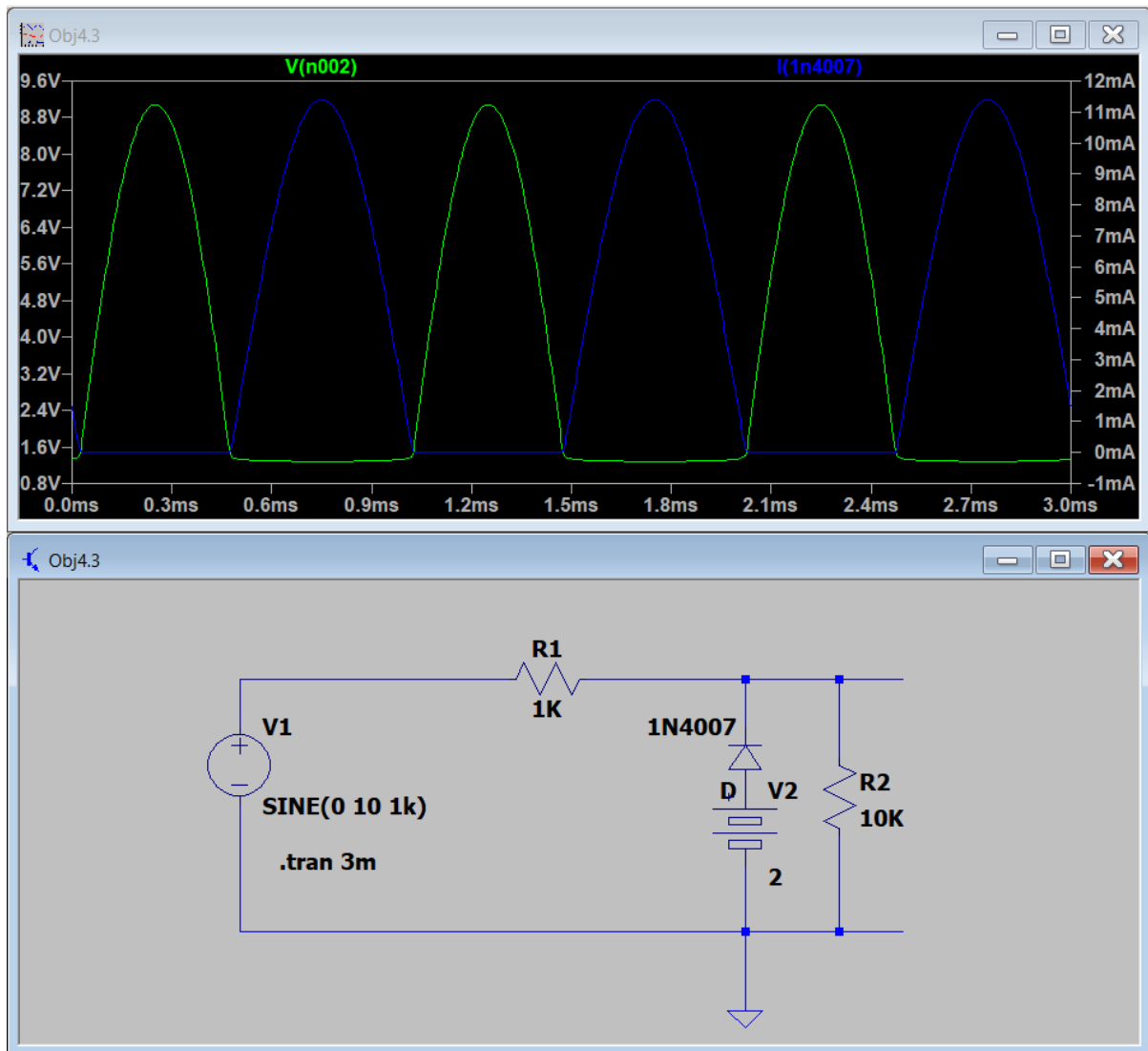

Case 3:

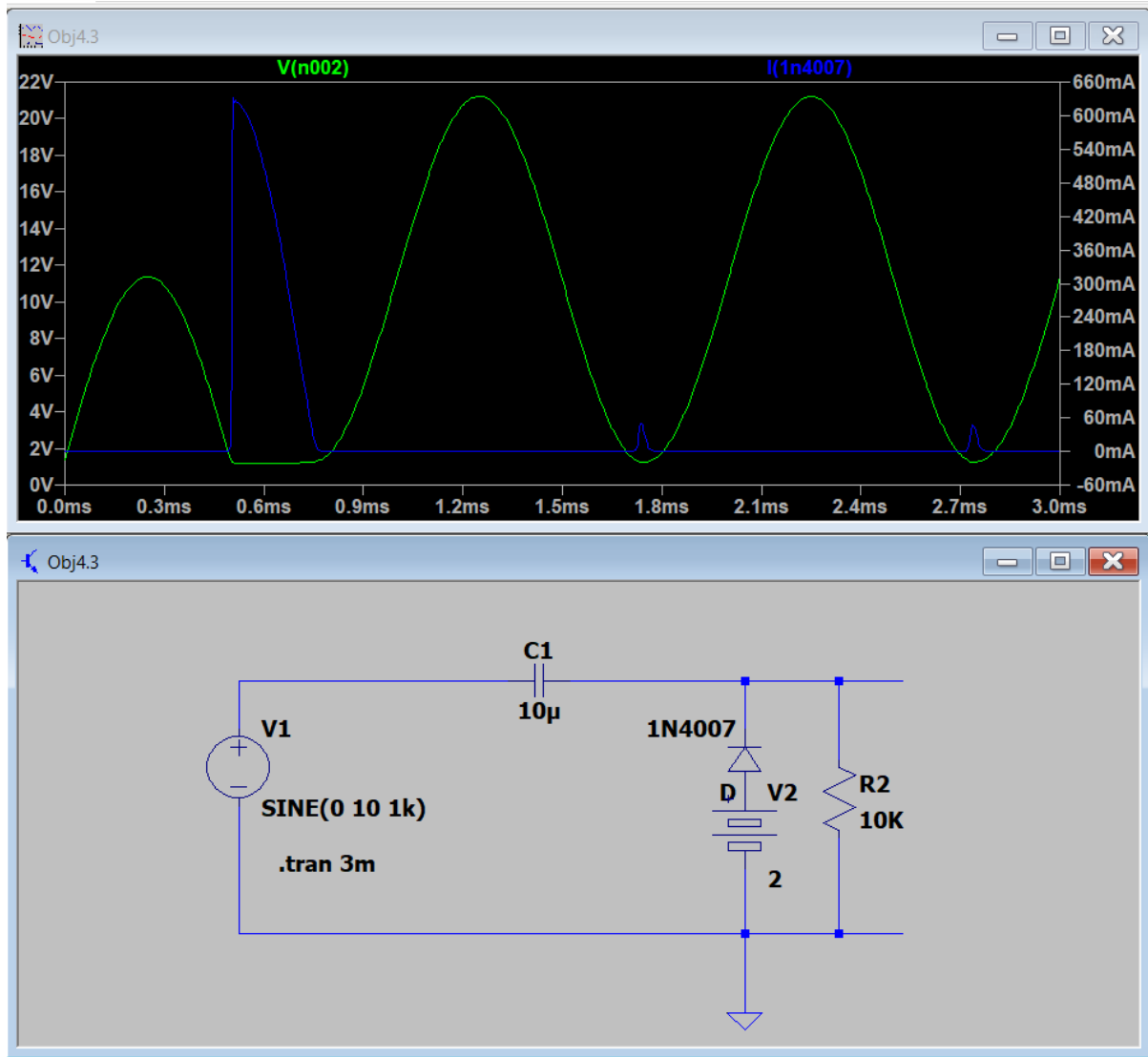

Case 4:

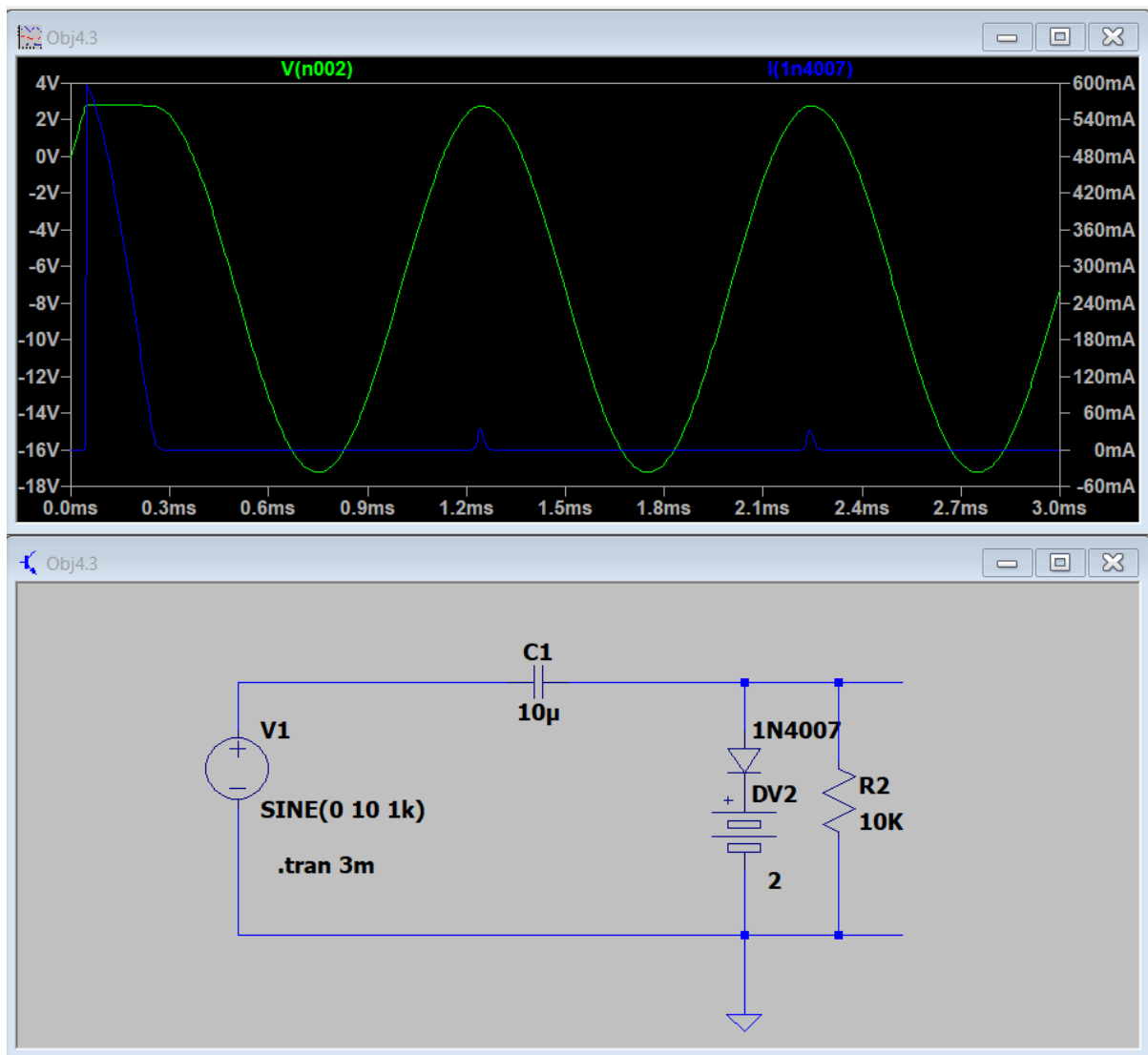

Discussion:

If the positive (negative) terminal of a voltage source is connected to P-side (N-side) of the diode then the diode is said to be in forward bias or ON, otherwise it is reverse biased or OFF. A real semiconductor diode made of Si needs approximately 0.7 V forward bias before it starts conducting current. In reverse bias, it conducts a negligible current which ideally should be zero. The forward current flows from p to n region.

The diode set-ups for the clipper and clamper circuits can be seen in the above schematics.

Clipping circuits are used to remove a part of a signal which is above or below a reference level. Clipping circuits are also known as limiters, amplitude selectors, or slicers.

In a clipper circuit, To alter the reference level to a desired value, a DC voltage source is put in series with the diode. Depending on the polarity of DC source and direction of diode the circuit will clip the input signal above or below the reference level set by the user.

A clamper circuit, on the other hand, shifts a signal to a defined value. Basically, this circuit adds a DC component to the input signal. The circuit can work with a bias or no-bias condition. If the signal shifts above the central line of a input wave, then it calls a positive clamper circuit and if it shifts downwards, then it is called a negative clamper circuit.