

Lab Report 4.1

Date: 21st September 2021

Name: Rita Abani

Roll No: 19244

Title of Experiment: Objective 3.1 : I-V characteristics of a diode.

Brief Description: In this experiment, we simulated a circuit in LTSpice to depict the I-V characteristics of a P-N Junction diode. A junction diode is basically a semiconductor PN junction made of p-type and n-type semiconducting regions.


An ideal diode is a perfect conductor for one direction of current whereas a perfect insulator for the opposite direction. However, in practice the diode does not behave as ideal conductor or insulator in any case. Diode is a unidirectional passive device and thus polarity of the power supply connected to a diode is an important factor that we need to consider especially for design and experimentation.

Schematic diagram:

We use a DC sweep set-up in linear mode and make observations regarding the resulting I-V waveforms across the diode.

To change the settings of the X-axis, we write V(n001)-V(n002) which is the voltage across the Diode.

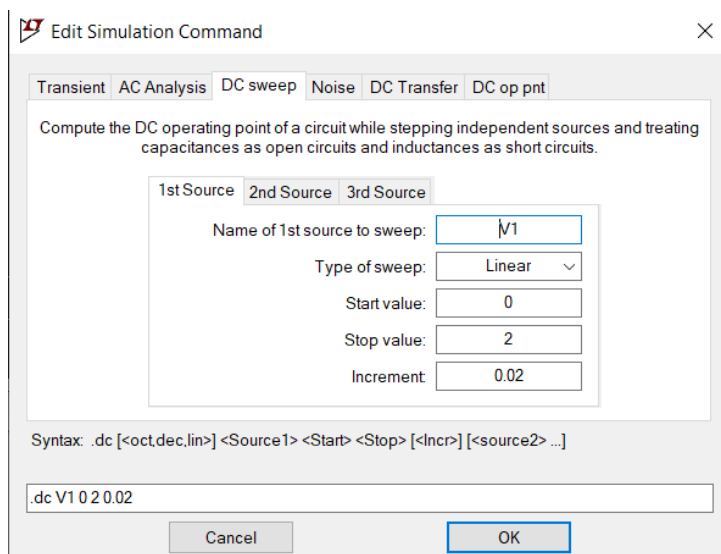We record both the Current across the diode and the Knee voltage




We use a DC sweep set-up in linear mode and make observations regarding the resulting I-V waveforms across the diode. We change the increment voltage 4 times to make eventful observations.


To change the settings of the X-axis, we write V(n001)-V(n002) which is the voltage across the Diode.

Following are the set-ups we considered:


Case 1: 5V

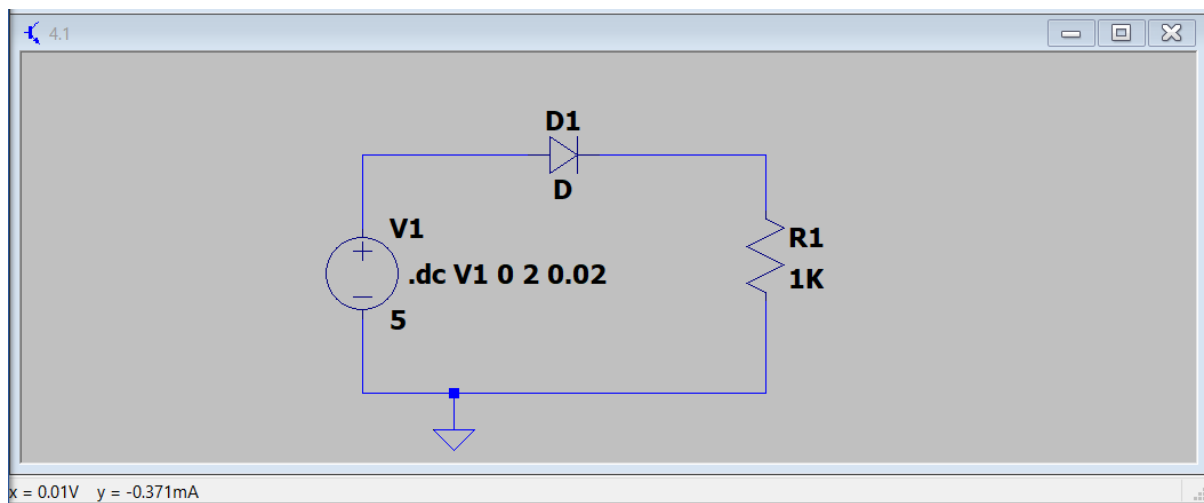


Case 2: 10V

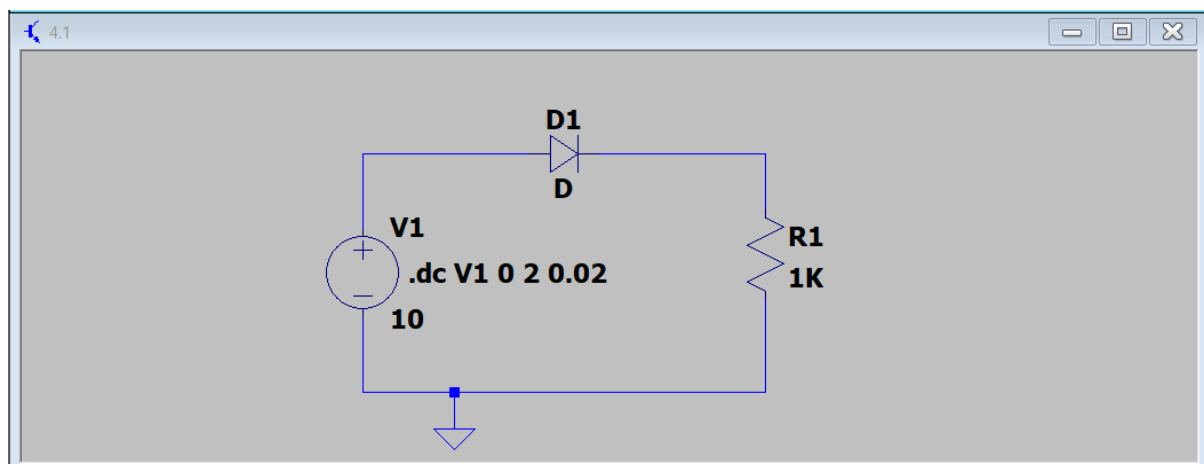

Case 3: 15V

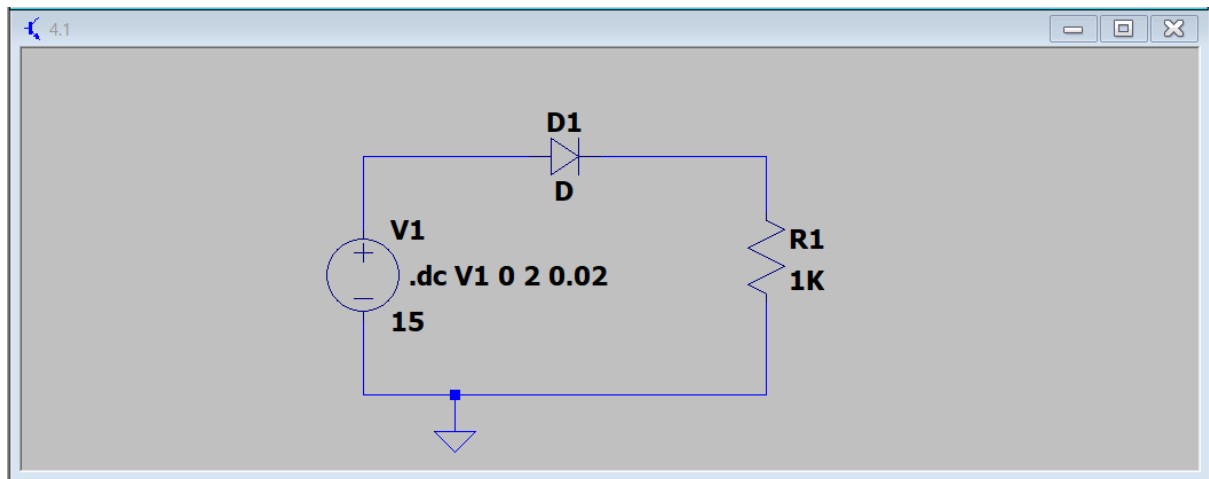

Case 4: 20V

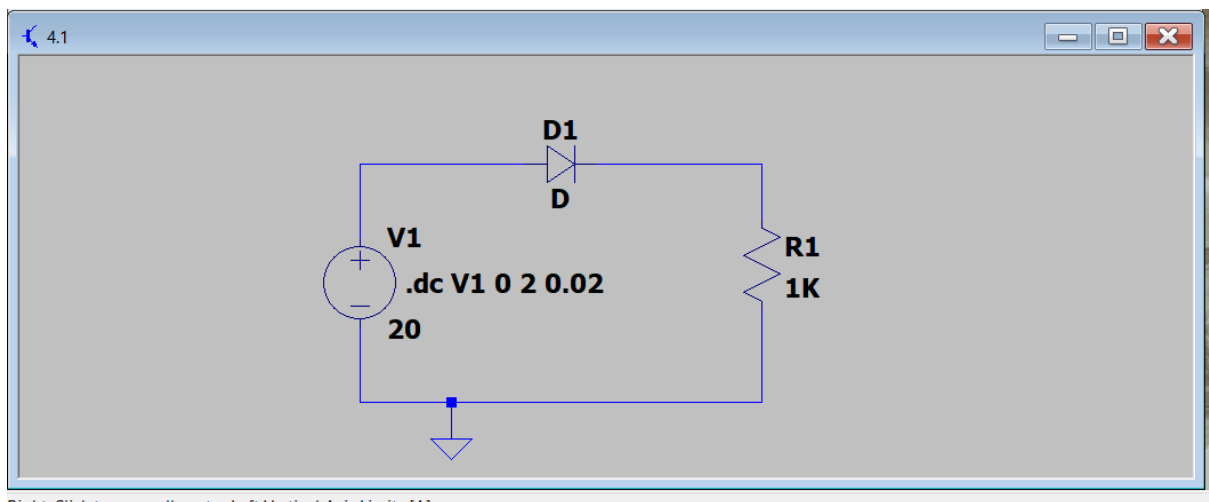

Results:

S.No	Supply Voltage (in V)	Diode Current (in mA)	Knee Voltage (in V)
1	5	1.328	0.66
2	10	1.332	0.67
3	15	1.324	0.66
4	20	1.326	0.66

Calculations:


Knee Voltage of the Diode = Average of the Knee voltages obtained in the above table

$$= (0.66 + 0.67 + 0.66 + 0.66) / 4$$


$$= 0.6625\text{V}$$

The following are the I-V characteristic curve obtained corresponding to each of the above cases


Case 1:

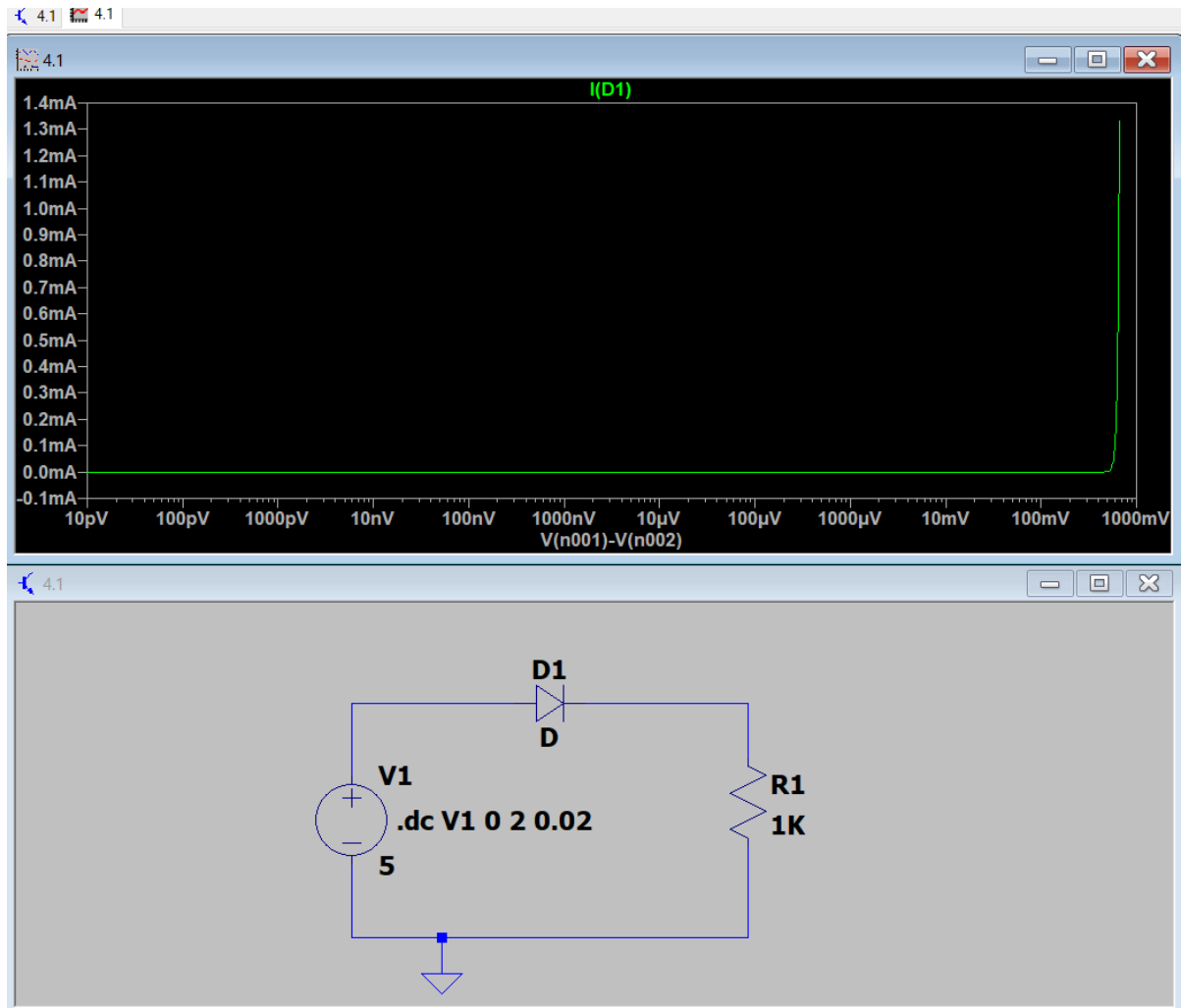


Case 2:

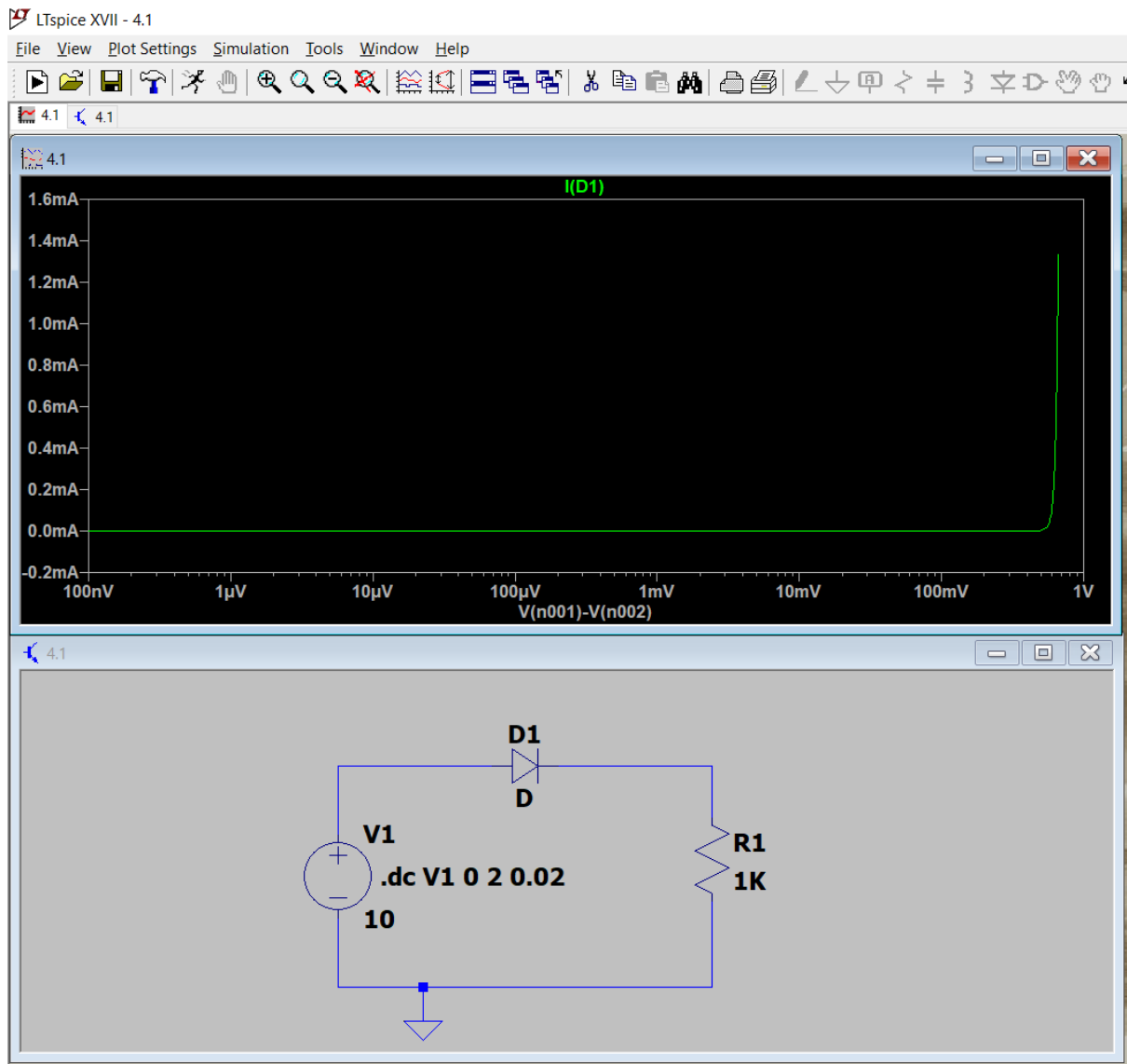

Case 3:

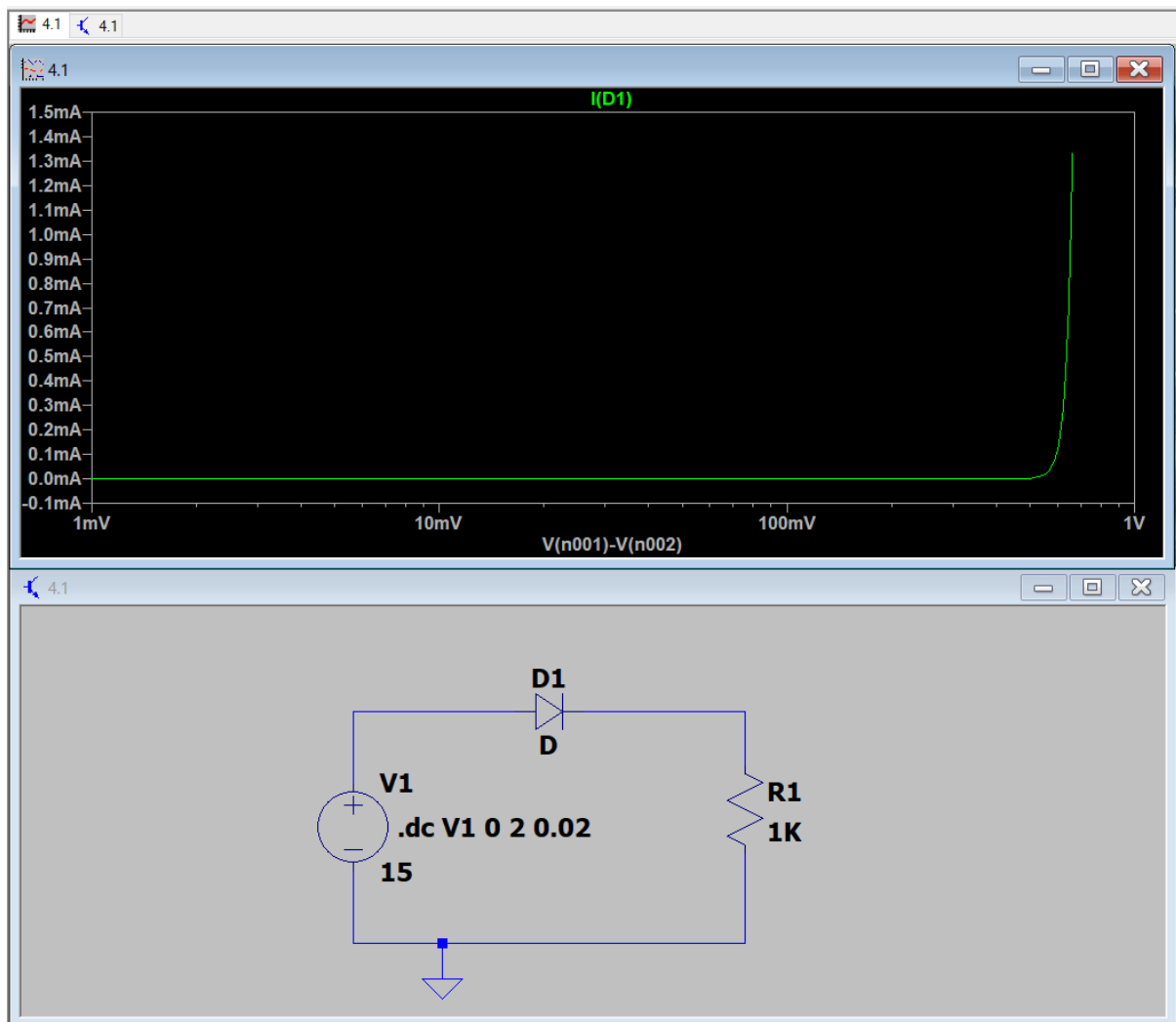

Case 4:

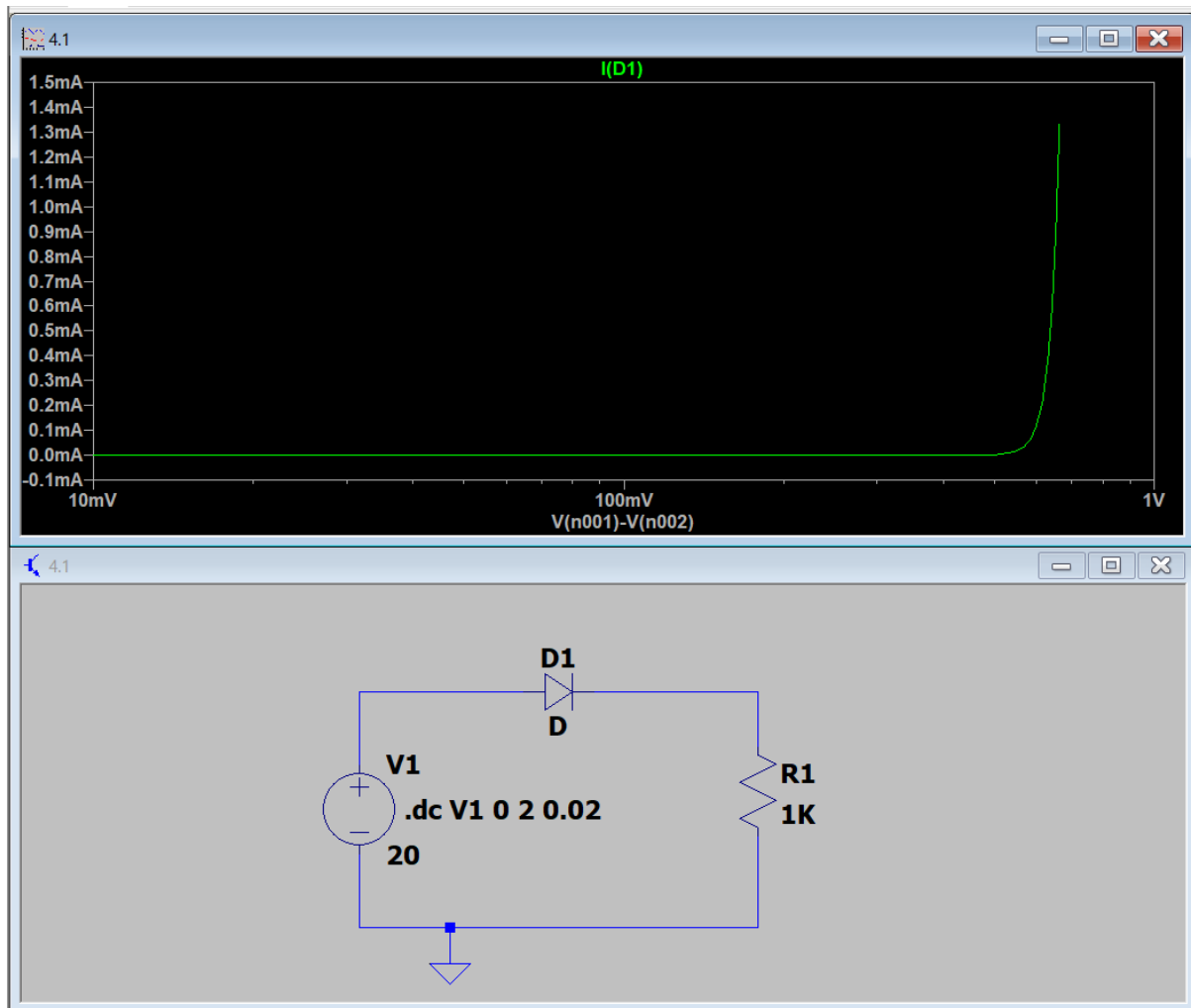

Discussion:

If the positive (negative) terminal of a voltage source is connected to P-side (N-side) of the diode then the diode is said to be in forward bias or ON, otherwise it is reverse biased or OFF. A real semiconductor diode made of Si needs approximately 0.7 V forward bias before it starts

conducting current. In reverse bias, it conducts a negligible current which ideally should be zero. The forward current flows from p to n region.

An ideal diode is a perfect conductor for one direction of current whereas a perfect insulator for the opposite direction. However, in practice the diode does not behave as ideal conductor or insulator in any case. A junction diode is basically a semiconductor PN junction made of p-type and n-type semiconducting regions.

We can express the current using the following formula: I_0

$$I = I_0 (e^{qV/KT} - 1)$$

Where:

I = the net current flowing through the diode;

I_0 = the diode leakage current density in the absence of light;

V = applied voltage across the terminals of the diode;

q = absolute value of electron charge

k = Boltzmann Constant and

T = absolute temperature (K).